

CPE-342 Microprocessor Systems and Interfacing

Min Project 1 (Group assignment. Maximum group size is 2)

Task 1: Controlling a 7-Segment display using a single I/O pin

Your task is to display numbers 0 to 9 with a delay of 2 seconds (approximate) between each number on a 7-segment display. You must only use a single I/O pin of the microcontroller to send data to the display. You will need to use additional circuitry to make this possible. You will do research to find a solution, test it in simulation using Proteus, then implement it in hardware on a bread board.

Restrictions:

You must only use a single I/O pin of the microcontroller to send data to the display. Other pins for control purposes may be used.

Task 2: Controlling four 7-segment displays using a single data bus

Your task is to display an arbitrary four-digit number on a set of four 7 – Segment displays. You must not use more than 10 I/O pins of your microcontroller for this task. You will do research to find a solution, test it in simulation using Proteus, then implement it in hardware on a perforated board (vero-board).

Restrictions:

- You may use up to 10 I/O pins of your MCU.
- 7-Segment display driver ICs are not allowed.

Deliverables:

- Proteus simulation of your designs for tasks 1 and 2. (3 marks)
- Code for the two tasks. (2 marks)
- Breadboard based hardware implementation for task 1. (5 marks)
- Vero-board based hardware implementation for task 2. (5 marks)
- A video showing the close-up of you soldering the vero-board. (2 marks)
- A report detailing your designs (including component selection), for tasks 1 and 2, the research you did to come up with solutions, and the problems you faced simulating and implementing them. (3 marks)

Submission Deadline: **Thursday 18th March 2021**

End of document
